

CSE 260M / ESE 260
Intro. To Digital Logic & Computer Design

Bill Siever
&
Michael Hall

This week

- Hw#4B due Wednesday
 - In-person demo required for full credit!
- Hw#5A posted tonight / due Sunday
 - A little shorter
 - In-person demo likely

RISC-V Edition of book!
RISC-V in the news...

Studio 4B Review & Ch 5


Studio 4B

- Full-Adder: Behavioral variations in simulation
 - iCE40 Mapping
- Full-Adder: Column of number


Ripple Adder

 - Example: 1111 + 0001
- As a traditional math problem:

$$\begin{array}{r} 1111 \\ + 0001 \\ \hline \end{array}$$



Info in circuit

 

- As values in a circuit:

0	0	0	0	<= Carry $i-1$ connected to carry in of i
1	1	1	1	<= "A"
0	0	0	1	<= "B"
0	0	0	0	<= "Sum"

Info in circuit: Initial

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 0 & 0 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{"A"} \\ + & 0 & 0 & 0 & 1 & \leq \text{"B"} \\ \hline 0 & 0 & 0 & 0 & \leq \text{"Sum"} \end{array}$$

Info in circuit: After 1st “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 0 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 1 & 1 & 1 & 0 & \leq \text{“Sum”} \end{array}$$

Info in circuit: After 2nd “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 0 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 1 & 1 & 0 & 0 & \leq \text{“Sum”} \end{array}$$

Info in circuit: After 3rd “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 1 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 1 & 0 & 0 & 0 & \leq \text{“Sum”} \end{array}$$

Info in circuit: After 3rd “Sum” update

- As values in a circuit:

$$\begin{array}{rcccc} 1 & 1 & 1 & 0 & \leq \text{Carry } i-1 \text{ connected to carry in of } i \\ 1 & 1 & 1 & 1 & \leq \text{“A”} \\ + & 0 & 0 & 0 & 1 & \leq \text{“B”} \\ \hline 0 & 0 & 0 & 0 & \leq \text{“Sum”} \end{array}$$

JLS Example: 1111+0001

Ripple Adder: Total Time

- N bits: Worst case scenario is ripple through all N
 - If T_c is the propagation delay through the Carry
= $N \cdot T_c$
 - Dictates things like maximum clock cycle for any paths/loops that use addition
 - Lots of things rely on addition!



Wikipedia Animation

**Studio 4B: Structural Ripple-Carry Adder
(And Generate Statement)
(And Hardware)**


Studio 4B: State Machines

Verilog FSMs

  - Three parts
 - Next state logic (arrows / next state table)
 - State register (active bubble)
 - Output logic (output equations)





Divide by 3 Counter

 


Verilog

```
module divideby3FSM(input  logic clk,  
                   input  logic reset,  
                   output logic q);  
  
    typedef enum logic [1:0] {S0, S1, S2} statetype;  
    statetype state, nextstate;  
  
    // state register  
    always_ff @(posedge clk, posedge reset)  
        if (reset) state <= S0;  
        else      state <= nextstate;  
  
    // next state logic  
    always_comb  
        case (state)  
            S0:    nextstate = S1;  
            S1:    nextstate = S2;  
            S2:    nextstate = S0;  
            default: nextstate = S0;  
        endcase  
  
    // output logic  
    assign q = (state == S0);  
endmodule
```

  

Chapter 5

Goal...and pattern...

 

$$**X = Y + Z**$$

(Using variables)

$$X = Y - Z$$

(Using variables)

$X = Y < Z$
(Using variables)

X = Y & Z
(Using variables)

Better (faster) Addition

Carry Look-Ahead

- Divide large addition into n -bit blocks
- Within each block, determine if what each column would with a carry-in to the column


- Would it “Generate” a carry? (g_x)

$$\begin{array}{r} ? \leq \text{Carry in} \\ a \leq \text{“A”} \\ + b \leq \text{“B”} \\ \hline s \leq \text{“Sum”} \end{array}$$


- Would it merely “Propagate” the carry? (p_x)

- Can the carry-out be represented in terms of a_x, b_x, cin_x, g_x and p_x ?

Building a Block (of 4)

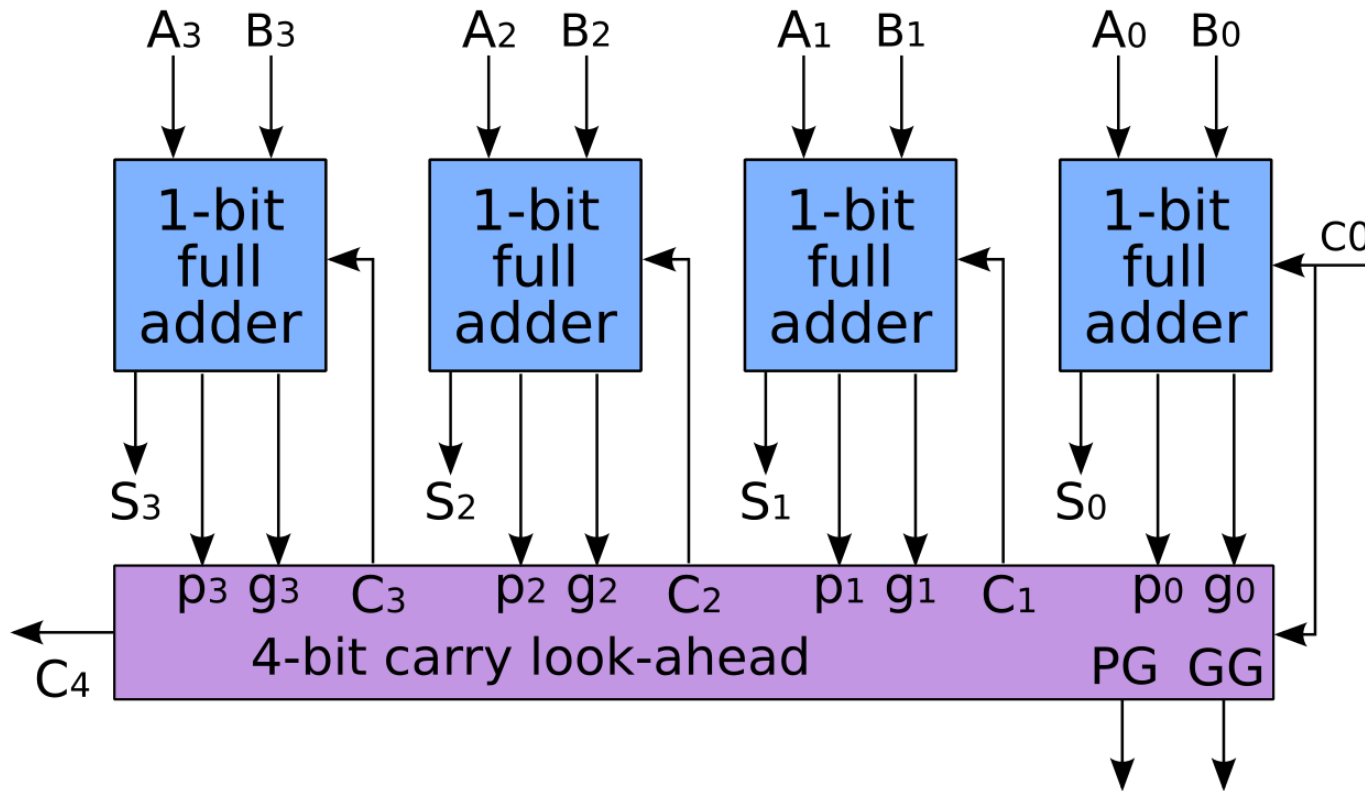


Extend “prediction” to block

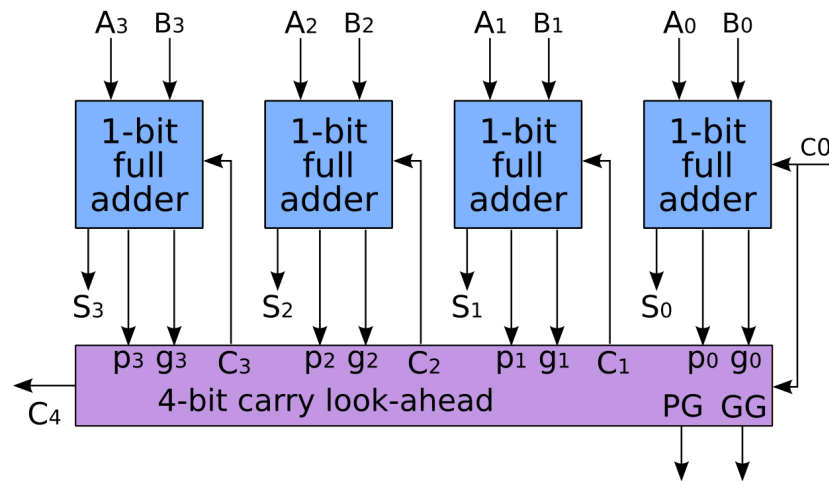


$$P_{block} = P_3 \cdot P_2 \cdot P_1 \cdot P_0$$

$$G_{block} = G_3 + P_3 \cdot (G_2 + (P_2 \cdot (P_1 \cdot G_0)))$$

Block “Prediction”

 

Ripple in 4 block, 16-bit CLA

 


Trade off: Logic vs. Time

- CLA and other tricks (Prefix adder) add logic to reduce time
- Degenerate Case: A look-up table (full sum-of-products equation)
 - How many layers of logic? (nots, ands, ors)?
 - To estimate complexity, how many rows and output columns are in a table to add two, 8-bit numbers?
 - Approximately how many AND gates?
Approximately how many OR gates?
Estimate the number of inputs that may be needed on OR gates

Subtraction

- The beauty of 2's complement


- $A - B = A + \bar{B} + 1$

 

Subtraction


- The beauty of 2's complement

- $A - B = A + \bar{B} + 1$

 

Comparisons

 - Equality
 - Easy: Are any bits different?
- Equal to zero?
- ?



Comparisons


- Less than (signed): Is $A < B$?
- Leverage Subtraction: $A < B$ is equivalent to $A - B < 0$
 - Subtract and check result
 - General: Is $A - B$ negative?
 - But...large numbers can “overflow”.
Need to consider overflow and signs of A & B

ALU: Arithmetic Logic Unit

- “Heart” of CPU: Does the computation stuff.

- Basic operations

 - Addition
- Subtraction
- Bitwise AND
- Bitwise OR
- Comparison (<)




ALU: Arithmetic Logic Unit

- “Heart” of CPU: Does the computation stuff.

- Basic operations

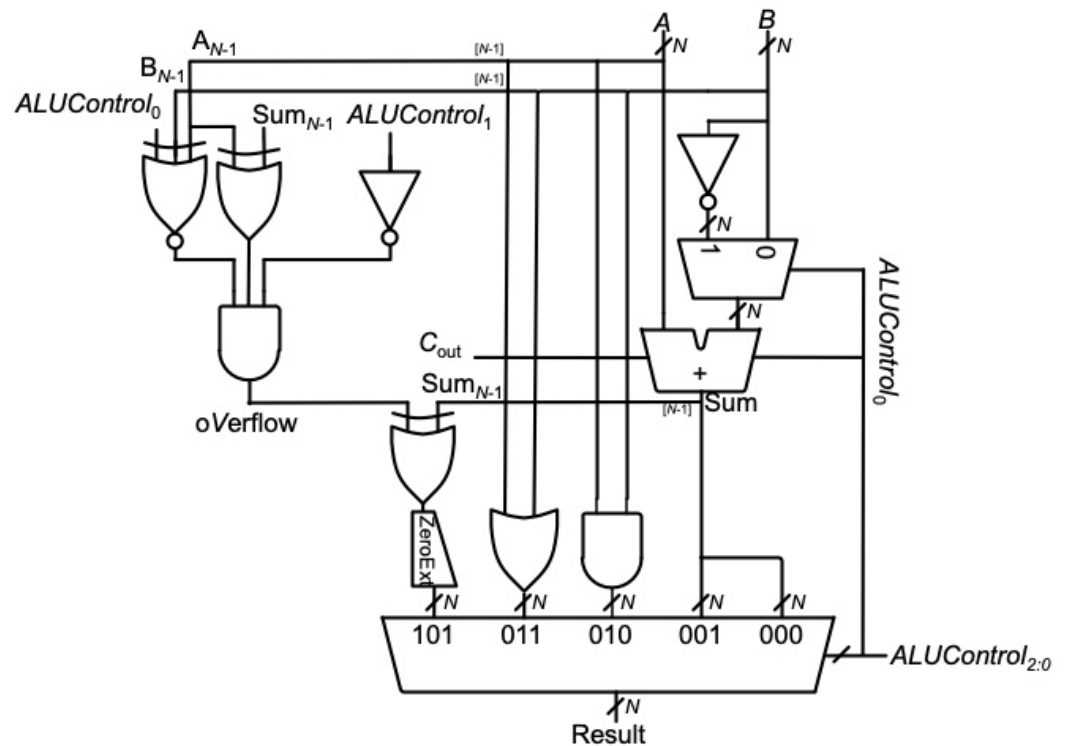- Addition: 000
- Subtraction: 001
- Bitwise AND: 010
- Bitwise OR: 011
- Comparison (<): 101



Other Operations: Shift Left (one place)

- $2^5 + 2^4 + 2^2 + 2^1 = 54$

Value	0	0	1	1	0	1	1	0
Place Value	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0

- $2^6 + 2^5 + 2^3 + 2^2 = 108$

Value	0	1	1	0	1	1	0	0
Place Value	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0

Shifting (unsigned / ∞ width)

- Left n bits: Equivalent to multiplication by 2^n
 - Multiplication algorithm is a mix of addition and multiplication by b^k
 - Ex: 123×12
 - Ex: $1011_2 \times 11_2$
- Right n bits: Equivalent to division by 2^n and truncation

Memory

Memory / Storage


- Common types
 - Static Random Access Memory (SRAM)
 - Dynamic Random Access Memory
 - Read Only Memory (contents can't be easily changed)

Memory / Storage

- General Approach
 - Store in a 2D grid of elements
 - Call each row a “word”
 - Each row has an index to access the content of the entire row

Memory Structure

 - One approach
- Bits are “enabled” to connect to shared output line




Memory / Storage

- Concept: Computer programming
 - An Array (List) is a representation of memory
- “Random” : Largely about time to access
 - The “random” means the location doesn’t have much impact on access time
- Vs. “Sequential”

Memory Structure

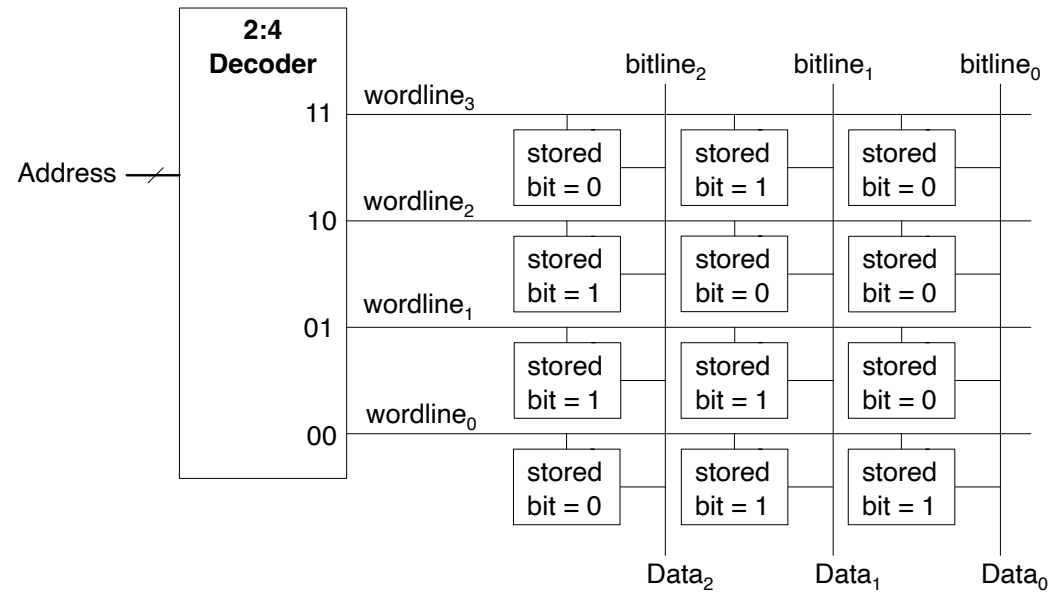- One approach
- Bits are “enabled” to connect to shared output line



A Sequential Example



RAM: SRAM vs. DRAM

SRAM vs. DRAM


- S = “Static”/Unchanging (well, only changing when requested!)
 - Could be built from D Flip Flops (but similar “self-reinforcing” circuits more likely)
- D = Dynamic: Values fade if not refreshed
- RAM: “Random Access”
 - About performance of reading/updating
 - Time take (*propagation delay*) does not depend on index requested

ROM

- Read Only
 - But still “Random Access” performance
- Fixed look-up table. Could be built with combinational logic!
 - Earlier example of “adder” could just be a ROM


Reading Memory

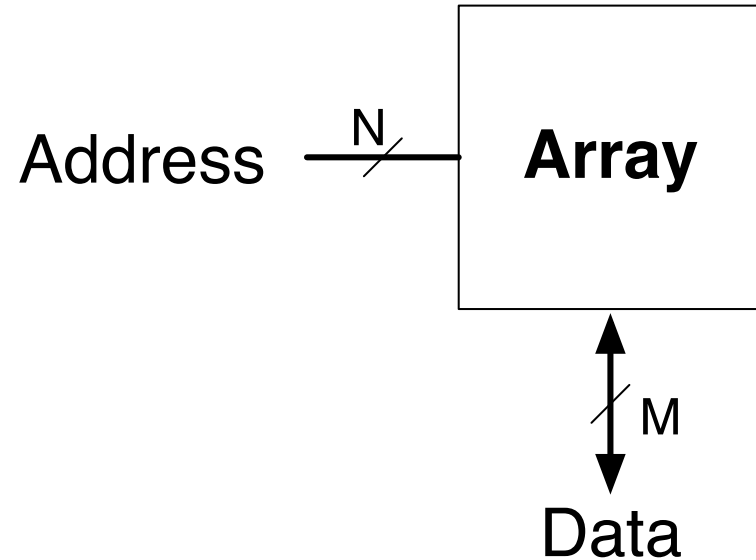- M = Word size
- N = “address size”
- How many total bits are stored?



ALU Operations

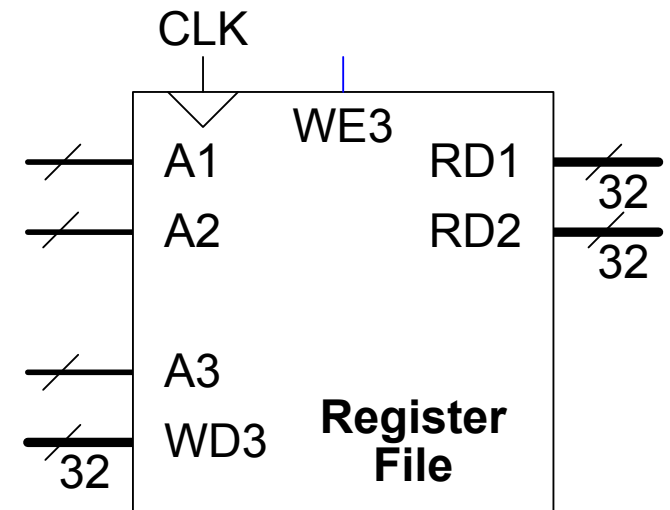- Context: $X=Y+Z$
 - We need places to hold Y, Z, and X.
- Need TWO inputs:
 - need a memory structure that provides 2 values (i.e. dual output ports)
- The “Register File”
- Also supports writing (updating)



JLS Register File (W/ D Flip Flops)

Verilog: RISC-V Register File


```
// 32 x 32 register file with 2 read, 1 write port
module regfile(input  logic      clk,
               input  logic      we3,
               input  logic [4:0] ra1, ra2, wa3,
               input  logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

    logic [31:0] rf[31:0];

    always_ff @(posedge clk)
        if (we3) rf[wa3] <= wd3;

    assign rd1 = rf[ra1];
    assign rd2 = rf[ra2];
endmodule
```

Big Picture: add x, y, z

 

FPGA

- Field Programmable
- Gate Array
 - Lattice iCE40 UP5k: Architecture Overview
 - RAMs, (Dual and Single Port)
 - Look Up Tables (LUTs): 4 inputs
 - D Flip Flops
 - Lots: ~5,000

Questions

- Chapter fits well with 361S
 - Wait until next chapter...
- Why so many memory types / what are the differences?
 - Evolution over time
 - Different needs: Capacity vs. Need — the memory hierarchy

Questions

- PLA vs. FPGA
 - PLA: (largely) 2-level logic / simple combinational logic
 - FPGA: Array of many programmable blocks with programmable interconnects
 - Can efficiently achieve more than 2-layer logic
 - Memory/storage is inherent (can do full state machine...see hw 4b)

